



Homework 03:

Student Name	
Student ID	
Section	
Dept.	
Year	
Date	

Question1. Draw the circuit diagram of a Traffic Light System using three LEDs (Red, Yellow, and Green) with Arduino. Clearly indicate the pin connections for each LED.

Question2: How can you add a buzzer that works only when the red LED is ON? Explain the required connections and write the necessary code snippet